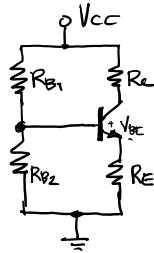


BJT Biasing


October 10, 2017 4:21 PM

Basic Bias Circuit:


- Used for common-emitter and common-base transistors.



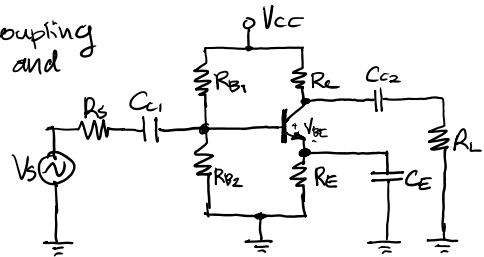With Bypass & Coupling Capacitors, load, and Source:



Thevenin Transformation:

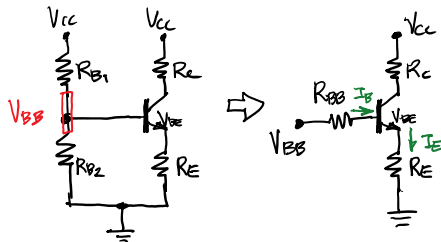

$$V_{BB} = V_{CC} \left(\frac{R_{B2}}{R_{B1} + R_{B2}} \right)$$

$$R_{BB} = R_{B1} \parallel R_{B2}$$


Using mesh analysis, we find I_B :

$$V_{BB} = I_B \cdot R_{BB} + V_{BE} + I_E \cdot R_E$$


$$I_E = (1 + \beta) I_B$$

$$\Rightarrow I_B = \frac{V_{BB} - V_{BE}}{(1 + \beta) R_E + R_{BB}}$$

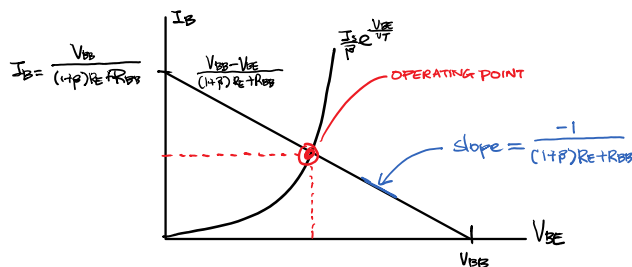Recall the relation: $I_B = \frac{I_C}{\beta} = \frac{I_S}{\beta} e^{\frac{V_{BE}}{V_T}}$, we plot the two and find operating point




Finding DC operating point

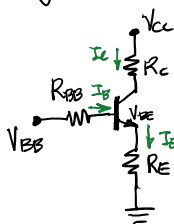


Start with mesh: $V_{CC} = I_C R_C + V_{CE} + I_E R_E$, $I_E = \frac{I_C}{\alpha}$


$$V_{CC} = I_C \left(R_C + \frac{R_E}{\alpha} \right) + V_{CE}$$
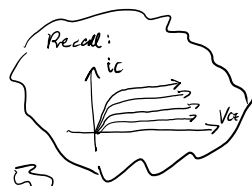
$$I_C \text{ as function of } V_{CE}: I_C = \frac{V_{CC} - V_{CE}}{\left(R_C + \frac{R_E}{\alpha} \right)}$$



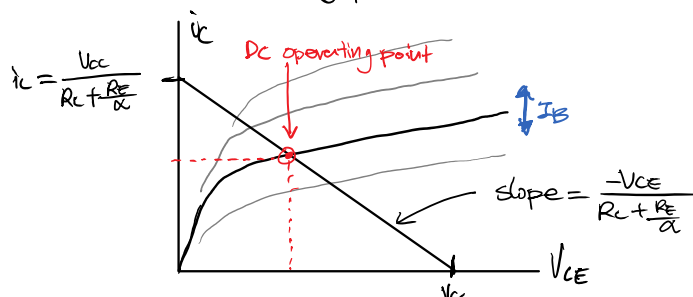
DC operating point is the intersection of I_C and characteristic curves



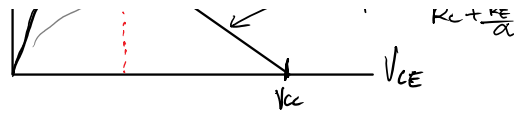


Finding AC Operating Point.

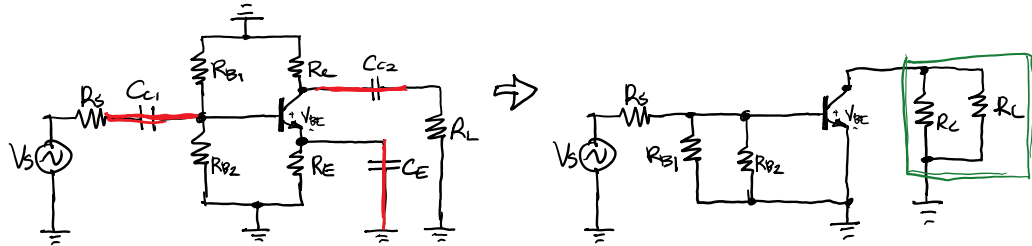
In AC small signal model, DC sources $\rightarrow 0$
capacitors $\rightarrow SC$



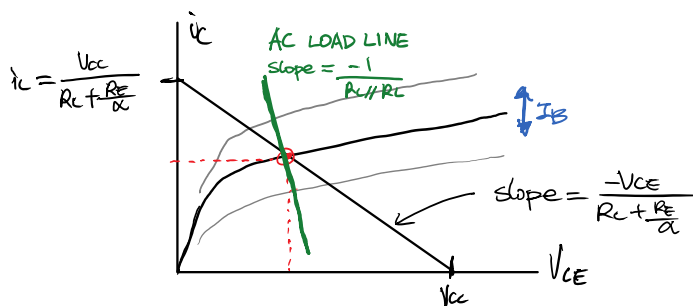Thus our load line is $\frac{-1}{R_C \parallel R_L}$




First Version of the $\frac{1}{3}$ Rule:

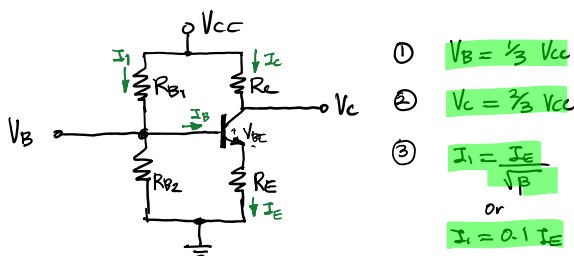


From the 3 rules, we proceed to calculate.

- $I_C = \frac{V_{CC} - V_C}{R_C} = \frac{\frac{1}{3}V_{CC}}{R_C} \rightarrow R_C = \frac{V_{CC}}{3I_C}$
- $I_1 = \frac{I_E}{\sqrt{2}} = \frac{V_{CC} - V_B}{R_{B1}} = \frac{\frac{2}{3}V_{CC}}{R_{B1}} \rightarrow R_{B1} = \frac{2V_{CC}}{3I_1} = \frac{2V_{CC}\sqrt{2}}{3I_E}$
- $I_B = I_1 - \frac{V_B}{R_{B2}} = \frac{I_E}{\sqrt{2}} - \frac{V_B}{R_{B2}} = \frac{I_E}{\sqrt{2}} - \frac{\frac{1}{3}V_{CC}}{R_{B2}} \rightarrow R_{B2} = \frac{R_{B1}(1 - \frac{1}{\sqrt{2}})}{1}$
- $I_E = \frac{V_E}{R_E} = \frac{\frac{1}{3}V_{CC} - V_{BE}}{R_E} \rightarrow R_E = \frac{(\frac{1}{3}V_{CC} - V_{BE})}{I_E}$, usually $V_{BE} = 0.7V$

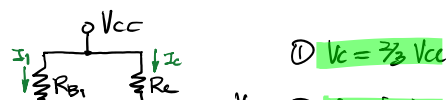Second Version of the $\frac{1}{3}$ Rule:



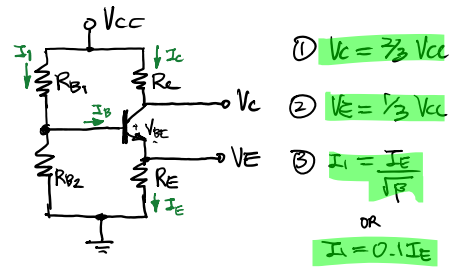

$$\rightarrow R_C = \frac{V_{CC} - V_C}{I_C} \approx R_E$$

$$\rightarrow R_{B1} = \frac{\frac{2}{3} V_{CC} - V_{BE}}{I_B / \beta}$$

$$\rightarrow R_{B2} = \frac{\frac{1}{3} V_{CC} + V_{BE}}{(\frac{1}{\beta} - \frac{1}{\beta + 1}) I_E} \approx \frac{(\frac{1}{3} V_{CC} + V_{BE}) \sqrt{\beta}}{I_E} \text{ for large } \beta.$$

$$\text{Usually } V_{BE} = 0.7 \text{ V}$$